 


PERIPHERAL MODULES FOR BASIC COMPUTER

from an idea by J. Haudry

The 8052-based single-board process and control computer introduced in ⁽¹⁾ is a system designed with hardware expansion in mind. This article describes two modular input/output boards that are indispensable when the BASIC computer is to control digital or analogue peripherals.



Peripheral modules for BASIC computer.

Technical characteristics:

- Modular I/O system comprises one address decoder/interface, and one or more input and/or output modules.
- Parallel mounting of up to eight digital I/O modules.
- Analogue output module based on 10-bit DAC supplies accurate voltage for control applications.
- Voltage span: 0 to 10.23 V, programmable in 10 mV steps.
- Use of one or more analogue output modules restricts the maximum number of modules controlled by 1 address decoder/interface to 7.
- Maximum of 2 address decoder/interface boards enables control of up to 16 digital I/O modules, or 14 analogue output modules.
- Power: digital outputs sink up to 500 mA at 50 V. Maximum total dissipation of output driver: 2.25 W (dissipation is 0.5 W, for example, when 300 mA is supplied).

Just for those who do *not* know: the system described in reference ⁽¹⁾ is a single-board computer based on Intel's Type 8052AH-BASIC v1.1 microcontroller. As indicated by the type number, the computer can be programmed in BASIC. Programming is done with the aid of a dumb terminal (or a host computer running a terminal emulation program), and a bidirectional RS232 link to the BASIC computer. The system can run programs from an on-board EPROM, and is, therefore, ideal for small-scale process and control applications ('turnkey' systems). Interestingly, control software is written and debugged direct on the system, and loaded into EPROM by the CPU, i.e., without the need of an EPROM programmer.

The BASIC computer has been one of the most popular projects published over the last year or so in this magazine. Users have found it simple to build, program, and connect to existing equipment. The BASIC interpreter in the 8052AH-BASIC is relatively fast, and supports a number of extremely useful bit-manipulation commands. Machine code programming is also possible when the Intel reference guide is available. After our publishing of the 'bare bones' of the BASIC computer, many users have expressed a firm interest in input/output extensions for connection to the available bus. The modules described here are our answer to these requests. Readers may be interested to know that the modules are also compatible with a 8751-based autonomous input/output controller with RS232 interface, to be described in a forthcoming issue of this magazine.

nt
rs
transistor
ages have
The AT
figure of
5 dB, and
5 dB. The
as a noise
ed gain of
1 GHz of

• Laser
Road •
ophone O
utors out
1988 issue

und manu-
sed prod-
of Arrow
istribution
xiom will
ects. In the
rector of
ands on
D's Sales
hile Greg
nager, and
Executive

Turnpike
• High
Telephone

Functional description of the I/O modules

Two types of bus-connected module are described here:

- a bidirectional digital interface with 8 inputs and 8 buffered outputs;
- an analogue output module capable of supplying a highly accurate output voltage between 0 and +10.23 V, in steps of 10 mV.

Between the BASIC computer's bus and these modules sits a simple address decoder. The I/O modules are small units, and one address decoder allows parallel connection of up to 8 digital modules, or up to 7 modules when analogue and digital types are used simultaneously. The BASIC computer itself allows the connection of a maximum of two address decoders. The modular structure of the expanded BASIC computer is illustrated in the block diagram of Fig. 1. The address decoder provides a bus in the form of a flatcable, which runs from one I/O module to the next.

Address decoder for I/O modules

The circuit diagram of Fig. 2 shows the simplicity of the address decoder for the

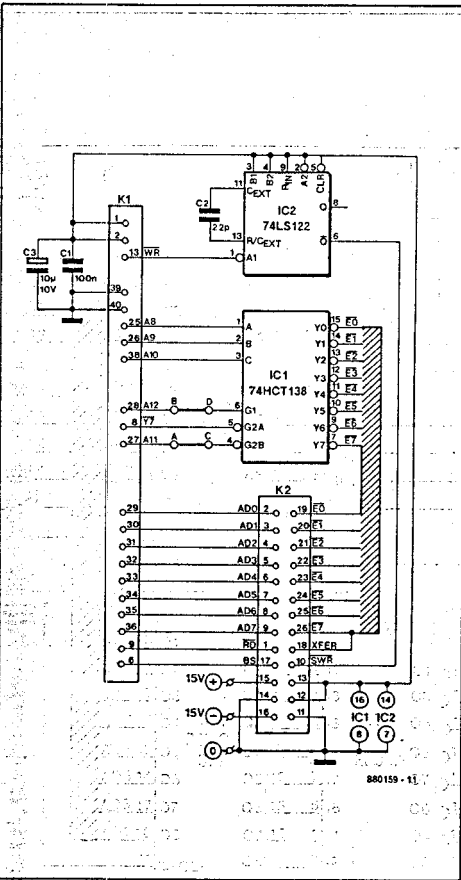


Fig. 2. The interface shared by the I/O modules is composed of an address decoder that divides the available memory space for I/O in 8 blocks of 256 addresses, and a circuit that modifies the timing of the WR pulse to ensure correct loading of the D-A converter.

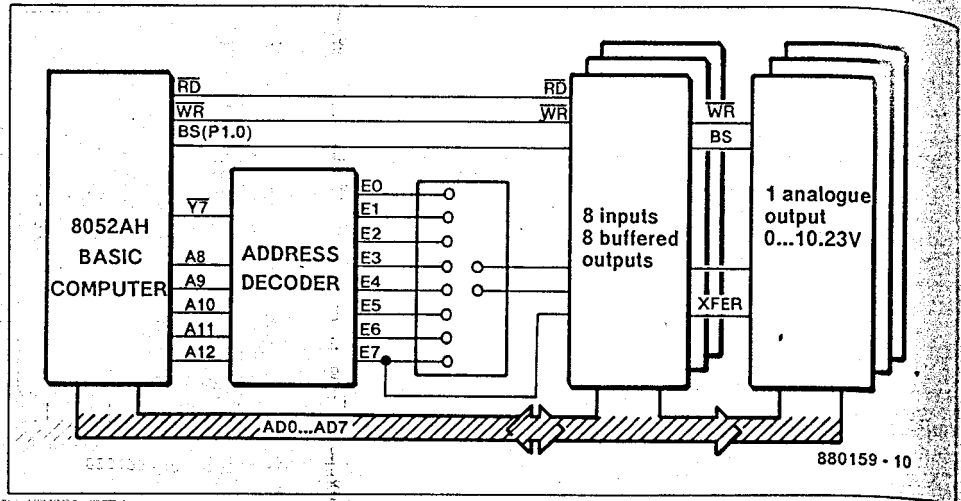


Fig. 1. The input/output system for the BASIC computer is a modular structure that gives the user freedom of configuration. The I/O boards are connected direct to the databus of the microcontroller, but are addressed in the memory segment reserved for peripheral circuits.

I/O modules. Monostable IC₂ is used for timing one of the control signals for the 10-bit digital-to-analogue (D-A) converter.

The presence of address lines A11 and A12 allows defining two address ranges, so that two decoders can be mounted in parallel, each with a different jumper configuration (A-D). Table 1 shows that each card occupies 256 addresses.

Address decoder IC₁ supplies 8 enable signals, E₀ to E₇. The special use of E₇ on the analogue output module will be reverted to, as well as the function of signal BS, which is supplied direct by the BASIC computer, and runs to the analogue output board(s) via the address decoder board.

Monostable IC₂ changes the timing of WR to provide a signal called SWR

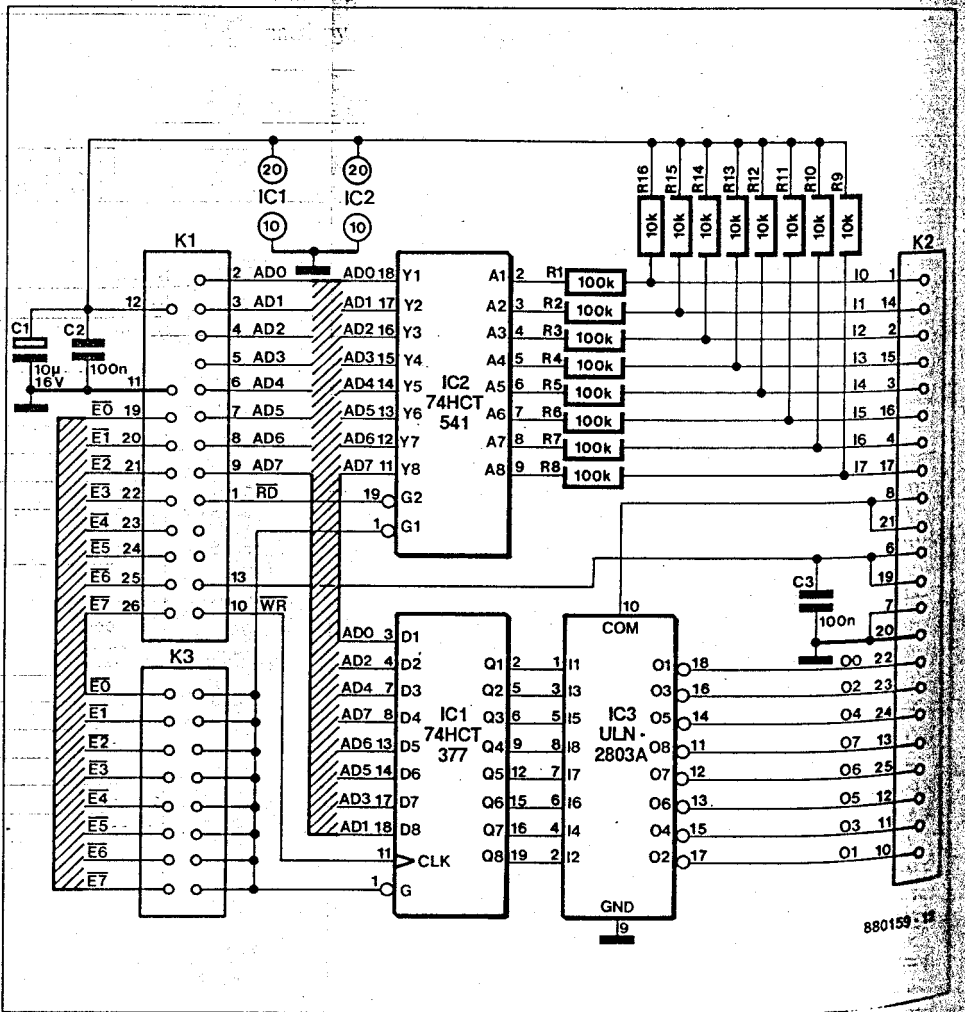


Fig. 3. Circuit diagram of the bidirectional digital interface. Up to 8 of these circuits can be controlled by a single address decoder.

short w
controlli
analogue
**Bidirec
output**
The circ
simple u
IC₁ is an
connecte
compute
the risin
signal, V
held logi
when the
puter fal
rump
When th
digital
rump
and jum
decoder

Circuit I
table line,
the read
roller.
example,
on K₃, an
decoder
roller to
E000 or
databyte
formed b

Fig. 4.
from Spr
Burlingto
Productiv

short write or special write), needed for controlling the D-A converter on the analog output module.

bidirectional digital input/output module

The circuit diagram of this basically simple unit is given in Fig. 3. Circuit IC₁ is an octal latch whose inputs are connected to the databus of the BASIC computer. Data is latched into IC₁ on the rising edge of the memory write signal, WR, but only when input \bar{G} is held logic low. This condition is satisfied when the address supplied by the computer falls within the range preset by the jumper on block K₃ (see Table 1.). When the processor writes a databyte to the digital output, e.g., at address F600H, jumper E6 should be installed on K₃, and jumpers BD and AC on the address decoder board (Fig. 2).

Circuit IC₂ is controlled by the same enable line, \bar{E}_x , as IC₁, and in addition by the read signal, RD, of the microcontroller. As a further configuration example, jumper E4 should be installed on K₃, and jumpers BC and AD on the decoder board, to enable the microcontroller to read a databyte at address EC00 on the digital I/O board. The databyte read by the selected card is formed by the logic configuration of the

Table 1. Address assignment of I/O modules.

Signal \bar{Y}_7 defines address range E000...FFFF, split in two by A11 and A12. Lines A8, A9 and A10 define 8 blocks of 256 addresses.

enable signal	wire links BD and AC	wire links BC and AD
\bar{E}_0	F000...F0FF	E800...E8FF
\bar{E}_1	F100...F1FF	E900...E9FF
\bar{E}_2	F200...F2FF	EA00...EAFF
\bar{E}_3	F300...F3FF	EB00...EBFF
\bar{E}_4	F400...F4FF	EC00...ECFF
\bar{E}_5	F500...F5FF	ED00...EDFF
\bar{E}_6	F600...F6FF	EE00...EEFF
\bar{E}_7	F700...F7FF	EF00...EFFF

All addresses in hexadecimal.

signals applied to inputs I0 to I7 on the 25-way D connector, K₂. Note that the input lines have pull-up resistors, so that any non-connected input is read as a logic high level. The pull-up resistors allow the digital input to be connected direct to an existing open-collector or open-drain output.

The Type ULN2803 in position IC₃ is an 8-way inverting power buffer composed of high-voltage, high-current darlington transistor arrays. This IC enables the digital output to directly control a wide range of loads, such as relays, solenoids, stepper motors and LED displays. Figures 4a and 4b show the inter-

 


Fig. 4. Internal diagram of the ULN2803 from Prague. Each of the 8 surge-protected darlington transistors in this chip can switch (inductive) loads of up to 500 mA.

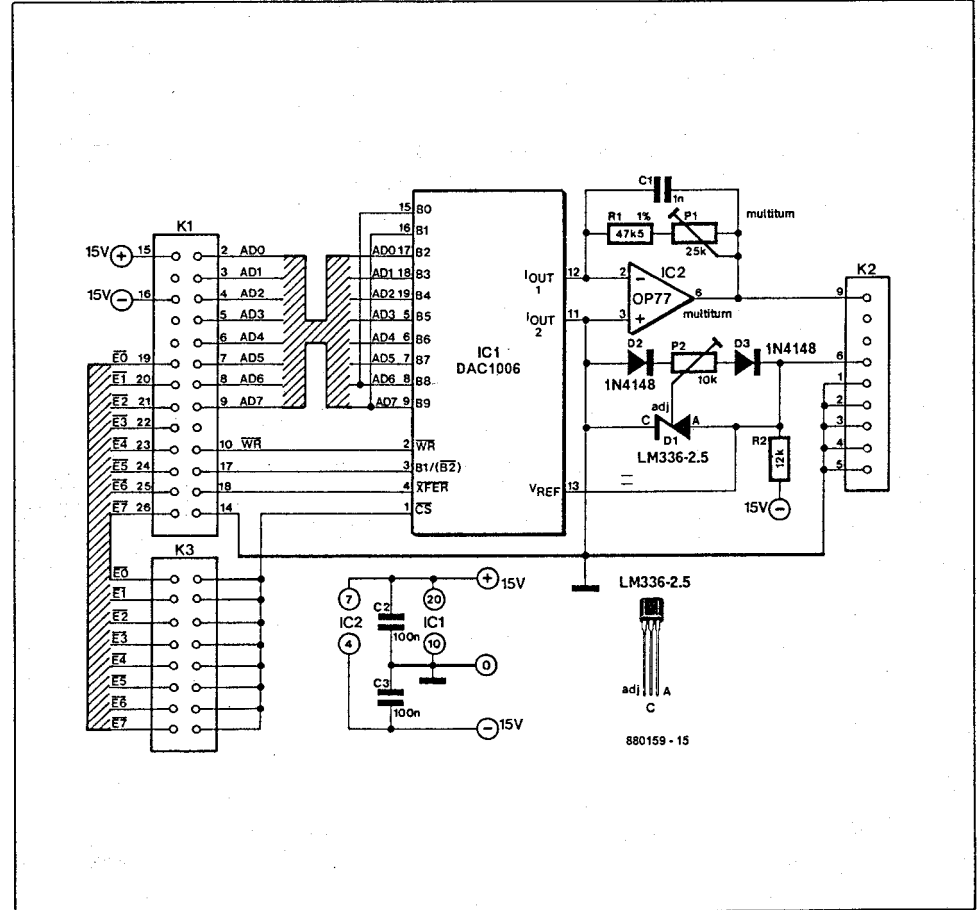


Fig. 5. The analogue output module is based around a 10-bit digital-to-analogue converter Type DAC1006 from National Semiconductor. The output voltage span is from 0 to 10.23 V in 10 mV steps.

nal structure of the ULN2803. Note that the buffers are of the inverting type, and that internal anti-surge diodes are provided to prevent damage to the open-collector output transistor when the current through the inductive load (relay coil) is interrupted. The anti-surge diodes are internally connected to a common rail, which is brought out to pin 10. This means that the supply voltage for the inductive loads controlled by the ULN2803 can be connected to pins 21 and 8 of K2.

Analogue output module

The heart of the D-A module shown in Fig. 5 is formed by IC₁, a Type DAC1006. This 10-bit DAC is remarkable for its excellent stability and capability to be controlled from an 8-bit bus. Loading of data (0 to 1023₁₀) is done in two successive operations, under

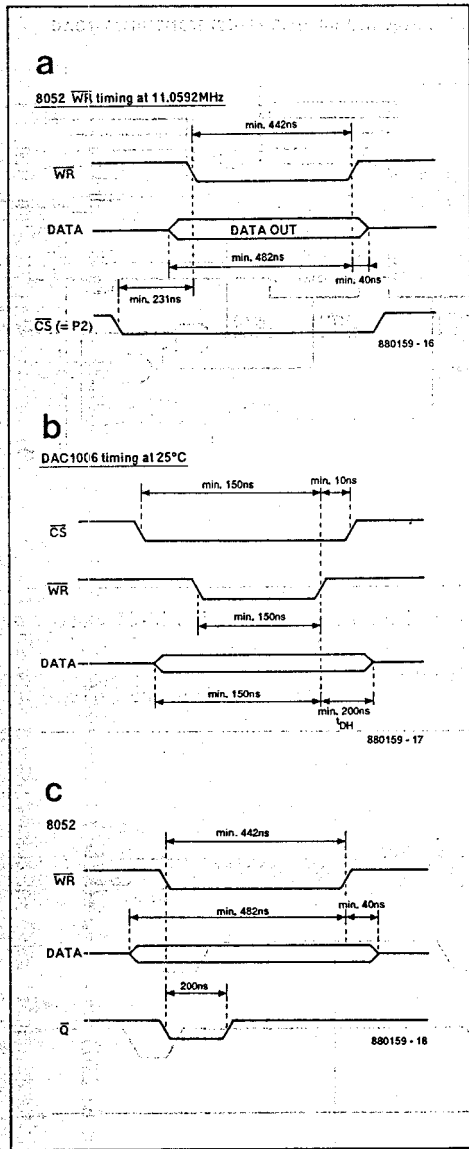


Fig. 6. For the DAC1006 to operate correctly, data should remain stable on the databus for at least 200 ns following the rising edge of the WR pulse (Fig. 6b), which is not so on the databus of the 8052AH-BASIC (Fig. 6a; $f_{CL} = 11.0592$ MHz). A monostable multivibrator is, therefore, required to shorten the WR pulse (Fig. 6c).

control of the logic level of the BS (byte select) signal applied to pin 3. This signal comes direct from the microcontroller 8052AH-BASIC via an output line of port P1. Users should decide for themselves which of these lines is to be used for providing signal BS. The Type DAC1006 has a few peculiarities which call for a rather special circuit configuration around it. Firstly, the DAC has a specific require-

ment as regards the duration of the databyte. The timing diagrams of Fig. 6 show that databytes are present on the bus for only 40 μ s after the WR pulse (Fig. 6a). The DAC1006, however, requires data to be present for at least 200 ns (Fig. 6b). This problem is solved by monostable IC₂ in the address decoder circuit (Fig. 2). Note that the 74LS122 used for this purpose is not available in the HCT version.

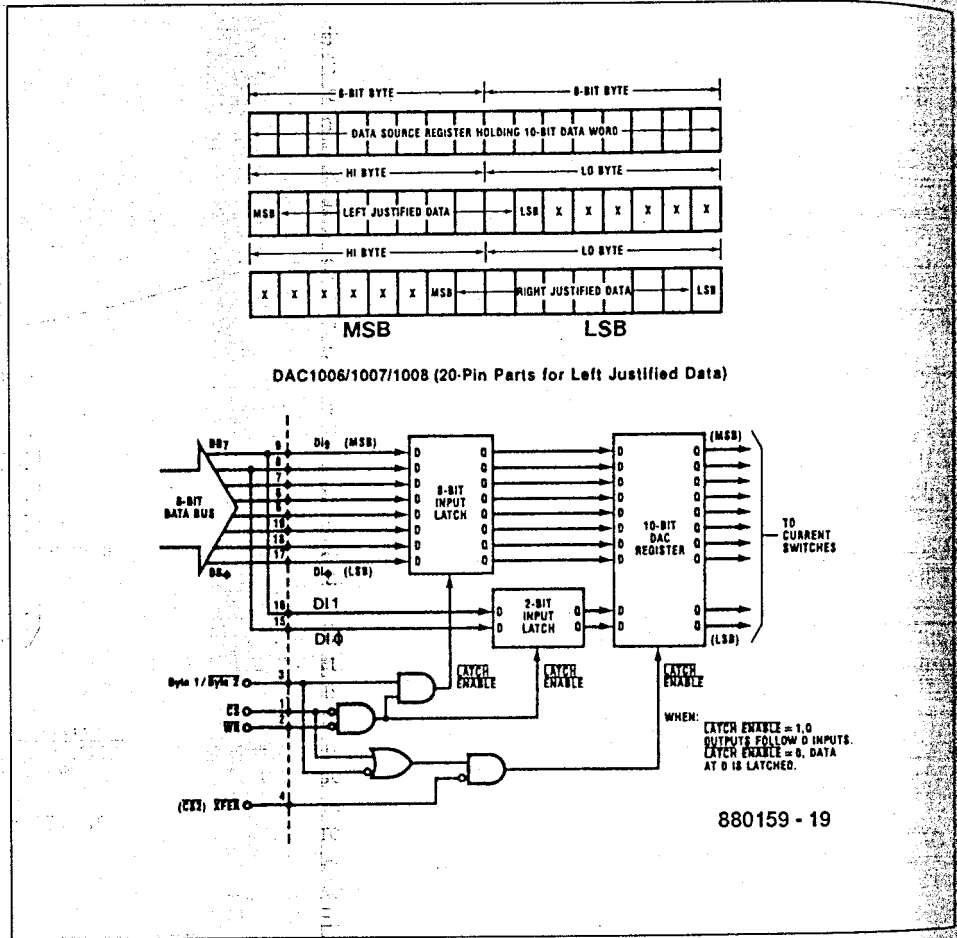


Fig. 7. The DAC1006 expects 10-bit, right-justified, data in a 16-bit databyte. Signal BS together with WR and CS, is needed to ensure that data from the 8-bit databus is sequentially latched into the device. A further signal, XFER, effects the transfer of the complete databyte from the latches to the internal conversion register.

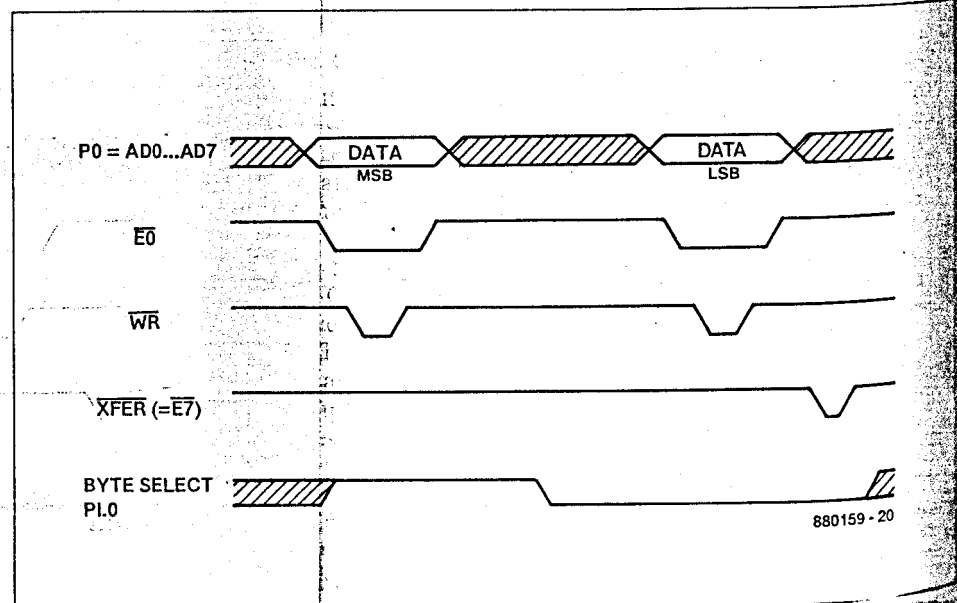


Fig. 8. Timing diagram relevant to the loading of data in the D-A converter.

Loadi
The se
DAC10
loaded
how si
the 10-
bits. U
are left
various
slightly
AD0 to
possible
mul
original
are load
remaini
also Fig
Once th
the lath
to the c
contr
simply
decoder
boards
decoder
output
line E7
digital
block th
convert
Figure 4
the sign
analog
E0, wh
P1.0 of
Smart y
for ad
one or
being u
insured
are cor
address
in the
= XF
using
The ex
DAC10
nal co
pensate

Adding the DAC

of the Fig. 6 on the R pulse per, re- at least solved address that the is not

se and peculiarity of the Type DAC1006 has to do with the way it is loaded with digital data. Figure 7 shows signal BS allows the chip to latch a 10-bit dataword as 8, followed by 2. Unconventionally, the 10 databits are left-justified in 16 available bit locations. Fortunately, in spite of the slightly unusual configuration of lines 00 to AD7, and B0 to B9, it is still possible to achieve right-justified data multiplication of the right-justified original 10-bit data by 64. The first 8 bits are loaded when BS is logic high, the 2 remaining bits when BS is logic low (see Fig. 8).

Once the 10-bit dataword is available in the latches, it is ready to be transferred to the conversion register. This operation is controlled by signal XFER, which is simply \bar{E}_x supplied by the address decoder board. This explains why only 7 cards can be connected to the address decoder when one or more analogue output cards are being used. In that case, \bar{E}_7 is not available for enabling a digital I/O module because it serves to block the transfer of the databits to the conversion register in the DAC1006.

Figure 8 shows the time relation between the signals involved. As an example, the analogue output module is addressed by \bar{E}_7 while BS is provided by port line 10 of the 8052AH-BASIC.


Start users may still be able to use \bar{E}_7 for addressing an eighth card, even if one or more analogue output cards are being used. This is possible provided it is ensured that the contents of the latches are correct the moment the 8th card is addressed, and that the databyte written to the latch of the selected card by \bar{E}_7 (XFER) is correct also (refer to the timing in Table 2).

external reference voltage for the DAC1006 is provided by D_1 , whose thermal coefficient can be accurately compensated by preset P_2 .

From current to voltage

the output of IC₁ supplies a current which is converted to voltage in opamp OP-77. Preset P_1 allows defining the full-scale value of the output voltage. The use of a relatively expensive opamp Type OP-77, which achieves an offset voltage of only 50 μ s at an ambient temperature of 25° C, may be questioned given the chip size of 'only' 10 mV.

It could be argued that a more common available opamp with an external offset compensation resistor would give the same results as the OP-77. This is not so, however, because the external compensation resistor would have a fixed value, while the output resistance of the converter chip changes with every new digital value loaded, due to the different configuration of the internal R-2R ladder network.

 

With reference to the simplified diagram of Fig. 9, the effect of this change on the static accuracy of the I-V converter can be expressed as the magnitude of the error voltage, calculated from

$$\text{error voltage} = V_{os}(1 + R_F/R_o)$$

where R_o is a function of the digital value written to the DAC:

$R_o \approx 10 \text{ k}\Omega$ for more than 4 logic high bits;

$R_o \approx 30 \text{ k}\Omega$ for any single logic high bit.

Therefore, the offset gain varies as follows:

$$\text{code} = 0011111111: \\ V_{err1} = V_{os}(1 + 10^4/10^4) = 2V_{os}.$$

$$\text{code} = 010000000000: \\ V_{err2} = V_{os}(1 + 10^4/3 \times 10^4) = \frac{4}{3}V_{os}.$$

The error difference between these values is $\frac{2}{3}V_{os}$.

It will be evident from the above that the non-linearity of the output voltage is a function of the opamp's offset voltage. When this is low (OP-77), the maximum deviation is also low, although still dependent of the digital value written to the DAC.

Construction and alignment

The peripheral extension modules for the BASIC computer are three printed circuit boards (Figs. 10, 11 and 12) interconnected by a bus formed by flat ribbon cable. The layout of the boards is

such that the output connector, K_2 , can be fitted onto the equipment front panel, with the board mounted perpendicular to this at the inside. At the other end of the cards, a 26-way flatcable plugged into K_1 runs from one card to another, connecting all of these to the bus card, which is mounted on the BASIC computer. The total length of the cable should not exceed about 30 cm to prevent digital interference on the databus.

The address decoder/interface card can be fitted direct on to the BASIC computer board, and is connected to it by a short length of flat ribbon cable. On the computer board, connect pin 7 of IC₃ (address decoding signal \bar{Y}_7) to pin 8 of the 40-way connector (K_2). It is also necessary to choose the Port 1 line to


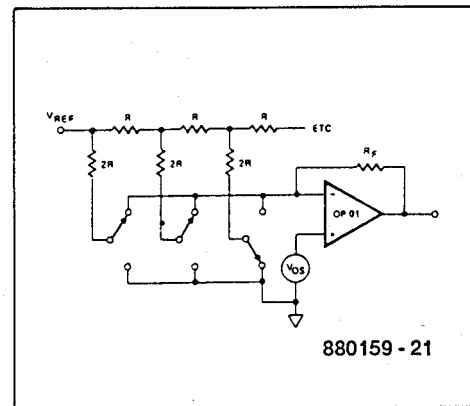


Fig. 9. Variation in output resistance of the DAC as a function of the converted code gives rise to a variable offset current at the input of the opamp, which translates current to voltage, and so magnifies the offset voltage. Obviously, the offset voltage of the opamp itself should be as low as possible.

 

Parts list
ADDRESS DECODER BOARD

Capacitors:
C1 = 100n
C2 = 22p
C3 = 10μ; 10 V

Semiconductors:
IC1 = 74HCT138
IC2 = 74LS122

Miscellaneous:
K1 = double-row 40-way right-angled header,
40-way right-angled male header with
handles.
K2 = double-row 26-way straight PCB header,
PCB Type 880159 (see Readers Services page)

Fig. 10. Printed circuit board for the address decoder.

supply BS. The connection between pin 6 of K₂ and pin 19 of K₁ shows that we have opted for Port 1 line P1. Any other line is equally suitable, as long as the software for the I/O modules takes this into account. If it is decided not to use the analogue output module, the last-mentioned link can be omitted. Similarly, the ±15 V supply is not required then.

The modules are ready after being assigned a memory address by placing a jumper on K₃.

There are only two, simple, adjustments to carry out on the analogue output board(s). First, correct the temperature coefficient of the LM336-2V5 by adjusting P₂ for a reference voltage of 2.490 V measured at pin 6 of the output connector, K₂. Next, write 1000₁₀ to the DAC (10 mV/LSB) and set the full-scale output voltage to 10.00 V with the aid of P₁.

The I/O modules discussed have a relatively low current consumption, and are, therefore, conveniently powered from the existing supply for the BASIC computer. The analogue board draws about 10 mA, the digital board and the decoder each about 20 mA.

Final notes

The contents of the conversion register in the DAC1006 are not defined at power-on, so that the output voltage may not be nought then. When an XFER pulse is received by a DAC, all other DACs connected respond to this

simultaneously. This means that the contents of the latches should correspond to the desired output voltage, which may not be the case at power-on. The analogue and digital ground lines may only be connected on the address decoder board.

Table 2. Examples of elementary command routines

For analogue module:

```

100 EO = 0F00H
110 XF = 0F700H
120 INPUT X
130 X = X * 64
140 PORT1 = 1
150 XBY(E0) = X/256
160 PORT1 = 0
170 XBY(E0) = X.AND.0FFH
180 XBY(XF) = 0
190 GOTO 120
    
```

```

REM output address (see K3)
REM dummy address (transfer)
REM get byte to convert
REM justify left
REM write byte
REM i.e. MSB, and then
REM LSB
REM (only bits 6 et 7 are useful)
REM clock 10-bit transfer
REM end of loop
    
```

For digital module:

```

10 E1 = 0F100H
20 Y = XBY(E1)
30 XBY(E1) = 00F3H
    
```

```

REM module address (see K3)
REM read input byte from Y
REM write byte F3
    
```

 


Fig. 11. Printed circuit board for the digital I/O module.

Parts list
DIGITAL I/O BOARD

Resistors:
R1...R8 incl. = 100K
R9...R16 incl. = 10K

Capacitors:
C1 = 10 μ ; 16 V
C2; C3 = 100n

Semiconductors:
IC1 = 74HCT377
IC2 = 74HCT541
IC3 = ULN2803A

Miscellaneous:
K1 = double-row 26-way right-angled header, or 26-way right-angled male header with eject handles.
K2 = 25-way D connector, male, with right-angled pins.
K3 = double-row 16-way straight PCB header.
1 jumper for mounting on K3.
PCB Type 880163 (see Readers Services page).

 


Fig. 12. Printed circuit board for the analogue output module.

Parts list
ANALOGUE OUTPUT BOARD

Resistors:
R1 = 47K5 1%
R2 = 12K
P1 = 25K or 22K multiturm preset
P2 = 10K multiturm preset

Capacitors:
C1 = 1n0
C2; C3 = 100n

Semiconductors:
D1 = LM336-2V5
D2; D3 = 1N4148
IC1 = DAC1006 (National Semiconductor)
IC2 = OP-77 (PMI)

Miscellaneous:
K1 = double-row 26-way right-angled header, or 26-way right-angled male header with eject handles.
K2 = 9-way D connector, male, with right-angled pins.
K3 = double-row 16-way straight PCB header.
1 jumper for mounting on K3.
PCB Type 880162 (see Readers Services page).

Reference:
(1) BASIC computer. *Elektor Electronics* November 1987, p. 24-31.

ader, or
th eject
ader.
page).

the con-
pond to
ch may
nd lines
address

u1)

When the logic outputs are used only for driving other digital circuits, the ULN2803 need not be fitted, and wire links may be installed between the PCB connections intended for the inputs and outputs of the chip.
Finally, do not forget that $\overline{E7}$ can not normally be used as a board selection signal because it is needed as XFER signal shared by the analogue output modules.