

Short Circuits

BENCH AMP



How it works

The gain of IC1 is set by the ratio $R9/R1 - 6$. Resistors $R1 - 6$ vary this from ≈ 20 to ≈ 0.5 . Thus to produce 100mV across $RV1$, inputs from 5mV to 200mV are required. $R7$ and $R8$ bias the non-inverting input to 4.5V and $R10$ is included to protect the chip. Since D.C. gain of the circuit is unity, the output will set at +4.5V D.C., providing maximum swing capability. To minimize output offset due to bias current, the value of $R7$ and $R8$ in parallel should be approximately the same value at $R9$. Bear this in mind if you intend to alter the supply voltage.



$R11$ and $C2$ provide decoupling for the 741 rail, as $C6$ does for the LM380. This capacitor can be increased in value to advantage with a supply not entirely stable. If another value of impedance speaker is employed, $R12$ will have to be altered to maintain the conditions.

THE AMPLIFIER TO BE described here differs in one major respect to most others - it can be used as an accurate millivoltmeter! One of the most awkward things to measure in a lab is an audio signal of less than a volt. Specialist meters are expensive, and rarely justifiable for an amateur: hence this project. This provides at least an 'order of magnitude' reading, and in most cases an accurate value can be assigned to the signal.

The circuit is basically an audio pre- and power amplifier combination, with switchable preamp gain. Depending on which sensitivity is selected, the gain of the 741 is so adjusted as to produce the specified input to drive the LM380 to the point of clipping. This voltage in turn is just sufficient to cause the LED to light.

To measure an A.C. signal, turn the volume control to maximum, and apply the input to the socket and work down from the lowest sensitivity until LED just comes on. The value of the input is now indicated by the switch. We tried several 380s and

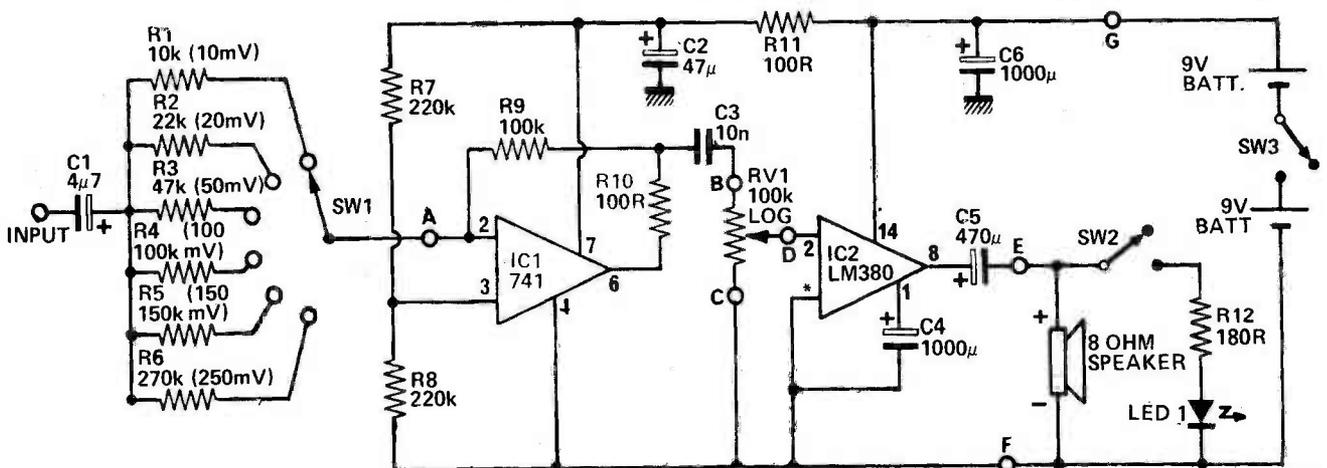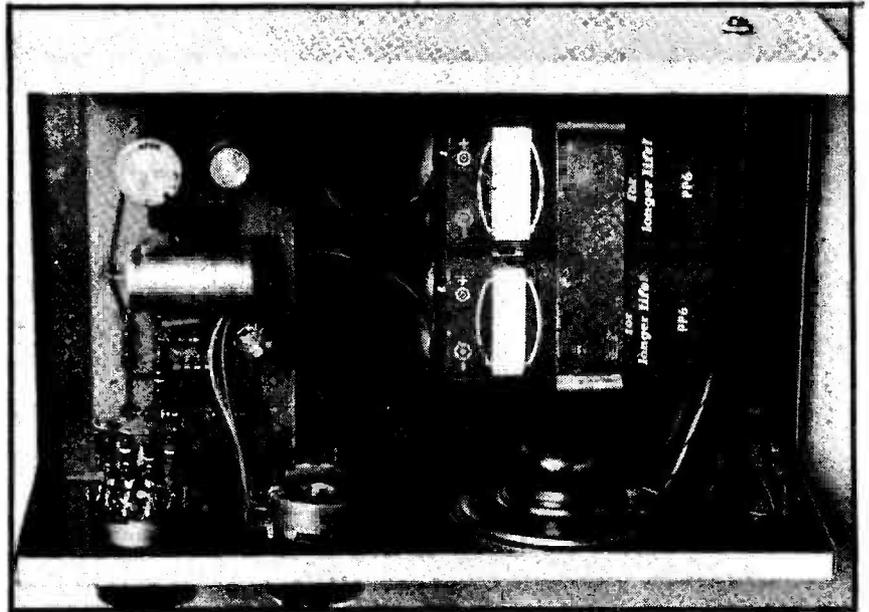several dozen LEDs to see if our results were repeatable: they were. In all cases we were within 10% of the value of the signal!




* PINS 3,4,5,7,10,11,12 ARE CONNECTED TO 0V

Circuit diagram of the Bench Amp

Construction is not critical, but a metal box is a good idea to help screen the amplifier from extraneous radiations etc. Ours came from Doram, and very nice they were too. Battery power was chosen so as to leave as much bench supply free as possible.


Further sensitivities can be easily added by using a larger switch with more poles, and adding the appropriate resistors. The quality of the circuit is good enough to feed an external loudspeaker, and a socket is provided to enable this to be accomplished. ●

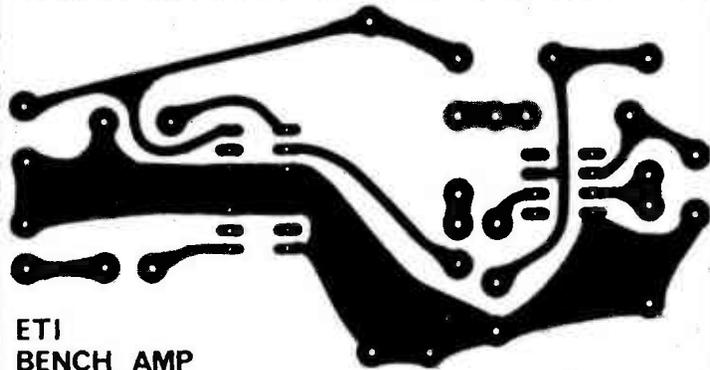

ET1
BENCH AMP

Parts List

RESISTORS		Nuts, bolts, etc.	
R1	10K	3.5mm jack socket	
R2	22K	CAPACITORS	
R3	47K	C1	4u7 16V electrolytic
R4,9	100K	C2	47u 16V electrolytic
R5	150K	C3	10n ceramic or similar
R6	270K	C4	1000u 16V electrolytic
R7,8	220K	C5	470u 16V electrolytic
R10,11	100R	C6	1000u 25V electrolytic
R12	180R	SWITCHES	
All 1/2W 5%		SW1	1 pole 6-way rotary
POTENTIOMETER		SW2	single pole / Off-On toggle
RV1	100K Log rotary	SW3	single pole / Off-On rocker
SEMICONDUCTORS		CASE	
IC1	741 op-amp	Samos S7	Doram
IC2	LM380 power amp	SPEAKER	
LED1	0.2" type	LS1	2 1/4" 8Ω type
MISCELLANEOUS			
Phono socket			

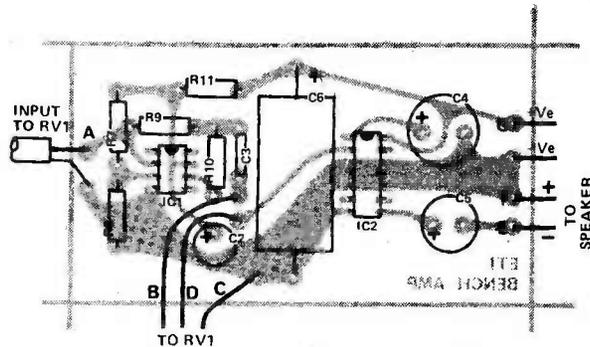

Component overlay for the Bench Amp



SUBSCRIPTIONS

Well, Mr. Quigley & Son may have got **THEIR Scanning Electron Printer working** but we are not **YET** sending ETI out on the Viewdata Link!

So if you can't get it from your newsagent, fill in the form below to ensure a regular copy — by post.

Help us to help you, please write your name and address on the back of your cheques.

To: **SUBSCRIPTIONS DEPARTMENT**
ETI MAGAZINE
25-27 Oxford Street
London W1R 1RF

ALL PAYMENTS MUST BE IN STERLING

I enclose £6.00 (£7.00 overseas) for the next twelve issues of ETI starting with the ... issue

Name

Address

Feb. '77